LITTLE WONDERS ESL

Science Word Lab: Electricity and circuits

Level B1 · about 25 minutes · batteries, wires and bulbs



1 BRAIN TEASERS

Read the clue. Write the English word in the boxes.

1. I store energy in a small case. I make a torch work. You can find me in a remote control. ☐☐☐☐☐☐☐
2. When you press me, you open or close a circuit. You use me to turn on a light. ☐☐☐☐☐☐
3. I am a material such as plastic or rubber. Electric current cannot flow through me. ☐☐☐☐☐☐☐☐

2 COOL FACT: A COMPLETE PATH

Electricity is a form of energy. It flows through a **circuit**, which is a complete path for electric **current**. A simple circuit has a **battery**, wires and a **bulb**. If there is a gap in the path, for example when a switch is open, the current stops and the bulb goes out. Metals such as copper are **conductors**, so current flows through them. Plastic and rubber are **insulators**, so they stop the current. Never touch sockets or wires at home, because mains electricity is dangerous.

flows = moves like water

gap = an empty space between two things

socket = the place in the wall where you plug in a machine

dangerous = not safe

3 WORD HUNT

Across or down

H	B	A	C	N	I	R	P	O	L	S	U
R	U	B	I	N	S	U	L	A	T	O	R
P	L	A	S	T	I	C	O	W	J	S	D
R	B	T	T	U	C	T	E	I	A	W	E
R	M	T	A	T	W	A	O	R	A	I	H
F	V	E	U	C	U	R	R	E	N	T	W
C	I	R	C	U	I	T	O	N	P	C	T
R	A	Y	O	S	N	U	S	E	C	H	L

WORD BANK

- ☐ **battery**
- ☐ **switch**
- ☐ **insulator**
- ☐ **circuit**
- ☐ **current**
- ☐ **bulb**
- ☐ **wire**
- ☐ **plastic**

4 SPEAK

Tell your teacher in your own words (about 1 minute)

1. What does a simple circuit have?
2. Why does the bulb go out when the switch is open?
3. Which materials are insulators?